ELEC6233 FPGA Implementation of a Complex Number Multiplier

Joshua Tyler jlt1e16 MSc Embedded Systems Dr Jeff Reeve

Abstract

1 Introduction

2 Design

Include 'Circuit diagrams' and discussion of design

 


Figure 1: Overall Block Diagram

- 2.1 Complex Multiplier
- 2.2 State Machine
- 3 Verification

Include sample data and results

 


Figure 2: Multiplier architecture

 


Figure 3: Read state machine state transition diagram

4 Synthesis

Include "Synthesis Result"

5 Conclusion

 


Figure 4: Main state machine state transition diagram

References